

## Karnaugh Maps (K-maps) - "Car-no"

Karnaugh maps were first applied to circuits in a 1953 paper

"The Map Method for Synthesis of Combinational Logic Circuits"  
by Maurice Karnaugh.

K-maps give us a graphical technique for the representation and simplification of a Boolean expression.

A Karnaugh map is made up of  $2^n$  boxes, representing the  $2^n$  entries of a truth table, arranged in a rectangular array (actually a torus would be more accurate). The correct positioning of the boxes is critical to the use of a Karnaugh map. Each box represents a binary sequence. Any two boxes which are adjacent horizontally or vertically must correspond to binary sequences differing in only one bit.

Example : 2 Variable K-map

B	A	0	1
		$\bar{A} \cdot \bar{B}$	$A\bar{B}$
0			
1		$\bar{A}B$	$AB$

Note: Each box represents a minterm. Each row a single term. Each column a single term.


Row 1 : represents  $\bar{B}$

Row 2 : represents  $B$

Column 1 : represents  $\bar{A}$

Column 2 : represents  $A$

Consider the circuit:

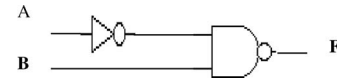

The corresponding truth table:

A	B	$\bar{A}$	$F = \bar{A}B$
0	0	1	0
0	1	1	1
1	0	0	0
1	1	0	0

Then we use the Karnaugh map by putting a 1 in a square which corresponds to 1 in the truth table.

B	A	0	1
		1 $\bar{A} \cdot \bar{B}$	1 $A\bar{B}$
0			
1		$\bar{A}B$	1 $AB$

We can now show F as a sum of minterms:

$$F = \bar{A}\bar{B} + A\bar{B} + AB$$

Indeed we can even easily represent F as a negation of a sum of minterms:

$$F = \bar{F} = \overline{\bar{A}\bar{B} + AB + AB} = \bar{A}\bar{B}$$

But the real power comes when we look at blocks of  $2^n$  entries.

B	A	0	1
		1	1
0			
1			1

The horizontal oval represents if  $B=0$  it doesn't matter what A is, we get a 1. This two-cell block is  $\bar{B}$ .

Likewise, the vertical oval represents if  $A=1$  it doesn't matter what B is, we get a 1. This two-cell block is  $A$ .

Using this reasoning,

$$F = A + \bar{B}$$

**Note :** This could have been done using *Algebra*

$$\begin{aligned} F &= \bar{A}\bar{B} + A\bar{B} + AB \\ &= (\bar{A} + A)\bar{B} + AB \\ &= \bar{B} + AB \quad \text{recall } (X + \bar{X}Y = X + Y) \\ &= \bar{B} + A \end{aligned}$$

## The 3-variable K-map:

C	AB	00	01	11	10
		$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
0					
1		$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

Individual cells represent minterms.

Blocks of two cells represent 2 term Products

Some examples:

C	AB	00	01	11	10
		$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
0					
1		$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

The oval represents  $\bar{A}\bar{B}$

		AB			
	C	00	01	11	10
0		$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}\bar{C}$	$A\bar{B}\bar{C}$	$A\bar{B}\bar{C}$
1		$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

The oval above represents  $\bar{B}\bar{C}$

		AB			
	C	00	01	11	10
0		$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}\bar{C}$	$A\bar{B}\bar{C}$	$A\bar{B}\bar{C}$
1		$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

The two corners represent  $\bar{B}\bar{C}$

Blocks of 4 cells represent individual variables (or their complements)

		AB			
	C	00	01	11	10
0		$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}\bar{C}$	$A\bar{B}\bar{C}$	$A\bar{B}\bar{C}$
1		$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

The 4 cells above represent  $\bar{A}$

		AB			
	C	00	01	11	10
0		$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}\bar{C}$	$A\bar{B}\bar{C}$	$A\bar{B}\bar{C}$
1		$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

The 4 cells above represent  $\bar{B}$

Lets use a Karnaugh map to help simplify

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C$$

		AB			
	C	00	01	11	10
0		$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}\bar{C}$	$A\bar{B}\bar{C}$	$A\bar{B}\bar{C}$
1		$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

We put ones in the corresponding positions:

		AB			
	C	00	01	11	10
0		$\bar{A}\bar{B}\bar{C}$ 1	$\bar{A}\bar{B}\bar{C}$ 1	$A\bar{B}\bar{C}$	$A\bar{B}\bar{C}$
1		$\bar{A}\bar{B}C$ 1	$\bar{A}BC$	$ABC$	$A\bar{B}C$ 1

Notice the vertical oval is not adding any new information. Adding its corresponding term will be redundant so we will omit it.

$$F = \bar{A}\bar{C} + \bar{B}C$$

For our last 3 variable example, consider reducing the function:

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C}$$

		AB			
	C	00	01	11	10
0		$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}\bar{C}$	$A\bar{B}\bar{C}$	$A\bar{B}\bar{C}$
1		$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

Putting the 1's in

		AB			
	C	00	01	11	10
0		$\bar{A}\bar{B}\bar{C}$ 1	$\bar{A}\bar{B}\bar{C}$	$A\bar{B}\bar{C}$	$A\bar{B}\bar{C}$
1		$\bar{A}\bar{B}C$	$\bar{A}BC$ 1	$ABC$	$A\bar{B}C$ 1

Notice there are not adjacent cells. This particular function can not be reduced.

#### 4 variable K-Map

CD \ AB	00		01		11		10	
	00	01	11	10	00	01	11	10
00	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}\bar{C}D$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$
01	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$A\bar{B}C\bar{D}$	$A\bar{B}CD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$
11	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$\bar{A}BC\bar{D}$	$\bar{A}BCD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$	$ABC\bar{D}$	$ABCD$
10	$\bar{A}BC\bar{D}$	$\bar{A}BCD$	$ABC\bar{D}$	$ABCD$	$A\bar{B}C\bar{D}$	$A\bar{B}CD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$

Individual cells represent minterms. 2 cell blocks represent 3 variable terms. 4 cell blocks represent 2 variable terms. 8 cell blocks represent 1 variable terms. (We only group  $2^k$  terms at a time)

Example: Use a K-map to simplify  $F = A\bar{B} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D + A\bar{B}\bar{C}\bar{D}$

We will start by identifying the appropriate cells –

CD \ AB	00		01		11		10	
	00	01	11	10	00	01	11	10
00	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}\bar{C}D$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$
01	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$A\bar{B}C\bar{D}$	$A\bar{B}CD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$
11	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$\bar{A}BC\bar{D}$	$\bar{A}BCD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$	$ABC\bar{D}$	$ABCD$
10	$\bar{A}BC\bar{D}$	$\bar{A}BCD$	$ABC\bar{D}$	$ABCD$	$A\bar{B}C\bar{D}$	$A\bar{B}CD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$

RULE OF THUMB: To achieve minimization include the smallest number of blocks having each having the largest possible number of cells.

CD \ AB	00		01		11		10	
	00	01	11	10	00	01	11	10
00	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}\bar{C}D$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$
01	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$A\bar{B}C\bar{D}$	$A\bar{B}CD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$
11	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$\bar{A}BC\bar{D}$	$\bar{A}BCD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$	$ABC\bar{D}$	$ABCD$
10	$\bar{A}BC\bar{D}$	$\bar{A}BCD$	$ABC\bar{D}$	$ABCD$	$A\bar{B}C\bar{D}$	$A\bar{B}CD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$

CD \ AB	00		01		11		10	
	00	01	11	10	00	01	11	10
00	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}\bar{C}D$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$
01	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$A\bar{B}C\bar{D}$	$A\bar{B}CD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$
11	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$\bar{A}BC\bar{D}$	$\bar{A}BCD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$	$ABC\bar{D}$	$ABCD$
10	$\bar{A}BC\bar{D}$	$\bar{A}BCD$	$ABC\bar{D}$	$ABCD$	$A\bar{B}C\bar{D}$	$A\bar{B}CD$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$

$$F = A\bar{C}\bar{D} + A\bar{B} + B\bar{D}$$